

Total No. of Questions :10]

SEAT No. :

P3608

[5560]-563

[Total No. of Pages : 2

**T.E. (Electrical)
POWER ELECTRONICS
(2015 Pattern) (Semester - I)**

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer any one questions from Q1 & Q2, Q3 & Q4, Q5 & Q6, Q7 & Q8, Q9 & Q10
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Black figures to the right indicate full marks.
- 4) Assume suitable data if necessary.

- Q1)** a) Explain with neat circuit diagram operation of R-C triggering circuit of Thyristor [5]
- b) Write short note on Class E Chopper. [5]

OR

- Q2)** a) Describe working of single phase semi converter with RL load. Draw waveforms of load voltage, load current. [5]
- b) Draw and explain output and transfer characteristics of MOSFET [5]
- Q3)** a) Describe working of single phase circulating type of dual converter with output voltage waveform. [5]
- b) State and explain different modes of operation of SCR with the help of V-I characteristic. [5]

OR

- Q4)** a) Explain the following ratings of the thyristor.
- i) Latching current
 - ii) Holding current [5]
- b) For a type A chopper circuit, source voltage $V_s = 220V$, chopping period, $T = 2000 \mu s$, on period $= 600 \mu s$, load circuit parameters: $R = 1\Omega, L = 5mH$ and $E = 24V$. Calculate the maximum and minimum values of steady state output current. [5]

P.T.O.

- Q5)** a) With neat diagram explain four mode operation of a TRIAC. [8]
b) Explain working of three phase fully controlled converter with RL load & firing angle of 30° . Draw output voltage waveforms & obtain expression for phase voltage & Line voltage. [8]

OR

- Q6)** a) A three phase full converter operating from three phase, 415V, 50Hz supply with resistive load, Determine average output voltage for $\alpha = 30^\circ$ and $\alpha = 90^\circ$. [8]
b) What is two stage ac voltage regulator? Explain its operation with output waveform for RL Load. [8]

- Q7)** a) For single pulse width modulation with quasi square wave show that output voltage can be expressed as
$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\pi}{2} \sin nd \sin n\omega t.$$
 Where V_s is source voltage and pulse width is $2d$. [8]

- b) Explain with circuit diagram and waveforms operation of single phase current source inverter. [8]

OR

- Q8)** a) Explain Sinusoidal Pulse width modulation with necessary waveforms. [8]
b) A single phase full bridge inverter is operated from 48V battery and is supplying power to a pure resistive load of 10Ω . Determine [8]
i) Output voltage (rms voltage)
ii) Output rms power

- Q9)** a) List different harmonic elimination techniques used in inverter. Explain any two methods in detail. [10]
b) Draw a neat diagram and explain cascaded multi level converter. [8]

OR

- Q10)** a) Explain working of three phase six step voltage source inverter in 180° mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. [10]
b) Write short note on Flying Capacitor multilevel converter. [8]

