

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5559]-203

S.E. (IT) (First Semester) EXAMINATION, 2019

DIGITAL ELECTRONICS AND LOGIC DESIGN

(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :- 1) Answer questions 1 or 2, 3 or 4, 5 or 6, and 7 or 8.

2) Neat diagrams must be drawn wherever necessary.

3) Assume suitable data, if necessary

1. (a) Convert given numbers in binary form and use 2's complement method to perform following operations [6]
i) $(-48) - (+23)$ ii) $(48) - (-23)$

- (b) Design and implement 8:1 MUX using two 4:1 mux and implement given function. [6]
 $F(X, Y, Z) = \sum m(1, 3, 4, 7)$

OR

2. (a) Explain with diagram CMOS to TTL interface [6]

- (b) Use K-map minimization technique to realize following expression using minimum number of gates. [6]
 $Y = \sum m(1, 2, 9, 10, 11, 14, 15)$

3. (a) Design MOD 93 counter using IC 7490. [6]

- (b) Draw and explain SISO and PIPO type of shift register. Give application of each. [6]

OR

4. (a) Draw JK Flip flop using gates and explain Race around condition with the help of timing diagram. [6]

- (b) A sequential digital system has input pin P and output Q. Output Q becomes 1 only when three consecutive '1's are received on pin P. Design the circuit using D flip flops and Moore modeling style. [6]

5. (a) Draw and explain general structure of PLA. [6]

- (b) Draw the ASM chart for 2 bit binary counter having enable input E such that if $E = 1$, counting enables and for $E = 0$ counting disables and starts from initial state. [7]

- (b) A sequential digital system has input pin P and output Q. Output Q becomes 1 only when three consecutive '1's are received on pin P. Design the circuit using D flip flops and Moore modeling style. [6]

- 5 (a) Draw and explain general structure of PLA. [6]
(b) Draw the ASM chart for 2 bit binary counter having enable input E such that if E =1, counting enables and for E =0 counting disables and starts from initial state. [7]

OR

- 6 (a) Implement following function using suitable PAL. $F(A,B,C,D) = \sum m(0,1,3,15)$ [7]
(b) Compare PROM, PLA and PLA devices. [6]

- 7 (a) Write VHDL code (Entity and Architecture) for 4:1 Multiplexer using Dataflow modeling style. [6]
(b) Explain structure of VHDL code and explain its various components. [7]

OR

- 8 (a) Compare Behavioural, Dataflow and Structural modeling styles in VHDL programming. [6]
(b) Write VHDL code for Half adder using Behavioural modeling style. [7]