

Total No. of Questions—4]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5216]-106

S.Y. B.Sc. (Computer Science) (I Sem.) EXAMINATION, 2017

ELECTRONICS

Paper II

ELC-212 : Analog Systems

(2013 PATTERN)

Time : Two Hours

Maximum Marks : 40

- N.B. :—**
- (i) All questions are compulsory.
 - (ii) Figures to the right indicate full marks.
 - (iii) Neat diagrams must be drawn wherever necessary.

1. Answer the following questions in *one* or *two* sentences each :

[10×1=10]

- (a) Define range of a sensor.
- (b) What do you mean by order of a filter ?
- (c) How many comparators are needed for a 8 bit simultaneous type ADC ?
- (d) Name the temperature sensor IC.
- (e) What is the role of a Wheatstone's Bridge as signal conditioner ?
- (f) Define resolution of a DAC.
- (g) Name any *two* passive transducers.
- (h) State any *one* application of pH sensor.
- (i) Draw frequency response of an ideal low pass filter.
- (j) Draw the circuit diagram for non-inverting amplifier using Opamp.

P.T.O.

2. Attempt any *two* of the following : [2×5=10]
- (a) Draw the neat block diagram of analog electronic system and explain function of each block.
 - (b) For a 3-bit Binary weighted resistor network ($0 = 0\text{ V}$, $1 = 5\text{ V}$). Find full scale output and output due to LSB change. What are the disadvantages of Binary weighted resistor network.
 - (c) Draw the circuit diagram of instrumentation amplifier using three opamp. Derive expression for its gain.
3. Attempt any *two* of the following : [2×5=10]
- (a) State working principle of ultrasonic sensor. State any *two* applications of ultrasonic sensor.
 - (b) Draw the circuit diagram of first order active high pass filter and explain its frequency response.
 - (c) Draw and explain Water Level Indicator System.
4. Attempt any *one* of the following : [1×10=10]
- (A) (i) Explain Dual Slope ADC with the help of neat diagram.
(ii) Differentiate between active and passive filter.
- Or*
- (B) (i) Explain working principle of capacitive type touch sensors. State any *two* applications where capacitive type touch sensors can be used.
(ii) With neat block diagram explain Intruder Detector system using PIR sensor.