

Total No. of Questions—4]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5116]-106

S.Y. B.Sc. (Computer Science)
(First Semester) EXAMINATION, 2017
ELECTRONICS
Paper II
(ELC-212 Analog Systems)
(2013 PATTERN)

Time : Two Hours

Maximum Marks : 40

- N.B. :—** (i) *All* questions are compulsory.
(ii) Figures to the right indicate full marks.
(iii) Neat diagrams must be drawn wherever necessary.

1. Answer all of the following in *one* or *two* sentences : [10×1=10]
- (a) Define the term 'Conversion time' with respect to ADC.
 - (b) For first order low pass filter calculate the cutoff frequency, if $R = 10 \text{ k ohm}$ and $C = 0.001 \text{ microfarad}$.
 - (c) Give any *two* examples of optical sensor.
 - (d) Define the term active sensor.
 - (e) Find output current of AD 590 at 300 degree Kelvin temperature.
 - (f) What is the use of Wheatstone's bridge circuit in signal conditioning ?

P.T.O.

- (g) Draw circuit diagram of op-amp as inverting amplifier.
- (h) What is advantage of R-2R ladder DAC over binary weighted resistor DAC ?
- (i) Write any *two* features of LM35.
- (j) State any *two* applications of tilt sensor.

2. Attempt any *two* of the following : [2×5=10]

- (a) Draw the circuit diagram of level shifter circuit and explain its working.
- (b) With suitable diagram explain operating principle of LVDT.
- (c) Draw circuit diagram of 4-bit R-2R ladder network DAC.

For a 4-bit R-2R ladder assume '0' = 0 volt and '1' = + 16 volts.

Find :

- (i) Full scale analog voltage.
- (ii) Analog voltage for 1011 digital input.
- (iii) Analog voltage due to LSB change.

3. Attempt any *two* of the following : [2×5=10]

- (a) Write the comparison between passive and active filters based on any *five* points.
- (b) Explain block diagram of intruder detector system using PIR sensor.
- (c) With neat block diagram explain the piezoelectric humidity sensor.

4. Attempt any *one* of the following : [1×10=10]

- (a) (i) Explain the block diagram of analog electronic system.
(ii) Draw circuit diagram of op-amp based voltage to frequency converter (VFC) and explain its working.

Or

- (b) (i) Explain the working of successive approximation ADC with neat diagram.
(ii) Draw simplified block diagram of ECG and explain its working.