



[4261] – 104

Seat No.	
-------------	--

**F.E. (Semester – I) Examination, 2012
BASIC ELECTRICAL ENGINEERING
(2008 Pattern)**

Time : 3 Hours

Max. Marks : 100

- Instructions :** 1) Attempt Q. No. 1 or 2, Q. No. 3 or 4, Q. No. 5 or 6, Q. No. 7 or 8, Q. No. 9 or 10, Q. No. 11 or 12.
2) Answer to the **two** Sections must be written **separate** answer-books.
3) Figures to the **right** indicate **full** marks.
4) **Use** of non-programmable pocket size scientific calculator is **permitted**.
5) **Neat** diagrams must be drawn **wherever** necessary.
6) Assume **suitable** data, **if necessary**.

SECTION – I

1. a) Define insulation resistance and obtain an expression for it of a single core cable. 8
- b) A motor pump set lifts 70 cubic meter of water per hour to a height of 40 meters. Efficiency of motor is 87% and that of pump is 83%. Find the monthly Bill for the use of set if it is used for 4 hours a day for 30 days. Cost of Electrical Energy is Rs. 10 per unit. 8

OR

2. a) If α_1 and α_2 are the resistance temp. coefficients at $t_1^\circ\text{C}$ and $t_2^\circ\text{C}$ respectively then prove that
- i) $\alpha_1 - \alpha_2 = \alpha_1\alpha_2(t_2 - t_1)$ and 8
- ii) $\alpha_1 / \alpha_2 = 1 + \alpha_1(t_2 - t_1)$
- b) An insulated cable has conductor diameter of 3 cm and insulation thickness of 2 cm. The resistivity of copper and insulation is $1.73 \times 10^{-8} \Omega - \text{m}$ and $9 \times 10^{12} \Omega - \text{m}$ respectively. Determine the resistance of conductor and insulator of the cable for 150 m length. 8

P.T.O.



3. a) Calculate the current flowing in the 10Ω resistance for the circuit shown in fig. 1 applying Kirchoff's laws. 10

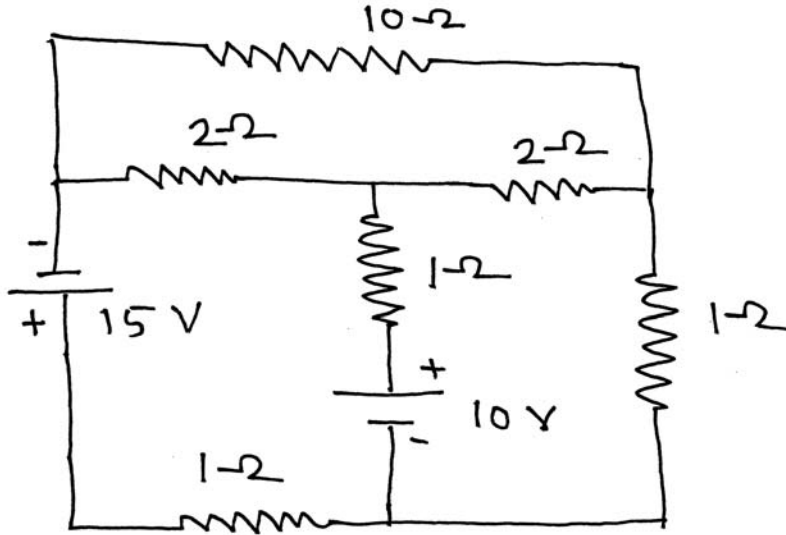


Fig.1 Q. 3(a)

- b) State and explain superposition theorem. 6

OR

4. a) Apply Thevenin's theorem to calculate the current flowing in 10Ω resistance for the circuit shown in Fig. 1. 10

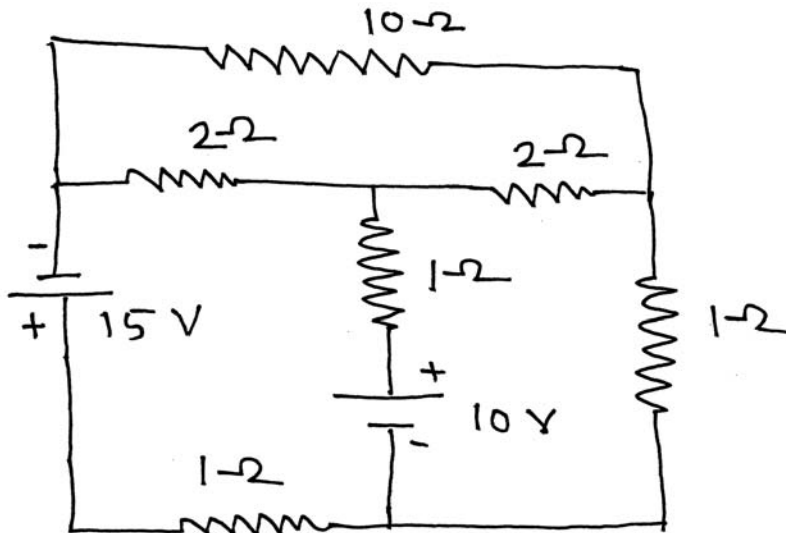


Fig.1 Q. 4(a)

- b) State and explain maximum power transfer theorem. 6



5. a) Compare Electric and Magnetic circuit. **6**
- b) Derive an expression for energy stored in the magnetic field. **6**
- c) Calculate the inductance of a toroid, 25 cm mean length and 6.25 cm^2 circular cross section, wound with 1000 turns of wire. Also calculate the emf induced when a current increasing at the rate of 200 A/s flows in the winding. **6**

OR

6. a) Define as ref. to magnetic circuit i) Magnetic flux, ii) Magnetic flux density
iii) Field strength iv) Reluctance and v) Permeance. **10**
- b) Draw a series magnetic circuit and parallel magnetic circuit also write down the expression for total Amp turns required ref. to both circuits. **8**

SECTION – II

7. a) Define R.M.S. value of sinusoidal quantity. Derive its expression in terms of peak value. **6**
- b) A potential difference of 11 KV is applied across a parallel plate capacitor with plate area of 0.01 m^2 separated by dielectric material 1 mm thick. The resulting capacitance of the arrangement is 300 pF. Calculate –
- i) Total electric charge
- ii) Electric flux density
- iii) Potential gradient
- iv) Relative permittivity of the dielectric. **5**



c) At $t = 0$, the instantaneous value of 60 Hz sinusoidal current is +5A and increases in magnitude further. Its rms value is 10 Amp.

i) Write the expression for its instantaneous value.

ii) Find the current at $t = 0.01$ sec.

iii) Sketch the waveform showing all values.

5

OR

8. a) Define average value of sinusoidal quantity. Derive its expression in terms of peak value.

6

b) A $12 \mu\text{F}$ capacitor is charged through $4 \text{ M}\Omega$ resistance from 120 V d.c. supply. Calculate

i) Time constant of circuit

ii) Time required for the voltage across the capacitor to reach 50 V

iii) Voltage across the capacitor 50 sec after closing the switch.

5

c) Three alternating currents are given by

$$i_1 = 150 \sin (\omega t + \frac{\pi}{4})$$

$$i_2 = 40 \sin (\omega t + \frac{\pi}{2})$$

$$i_3 = 80 \sin (\omega t - \frac{\pi}{6})$$

They are fed into a common conductor. Find the equation of resultant current.

Also find rms value of resultant current.

5



9. a) If a sinusoidal voltage $V = V_m \sin \omega t$ is applied across purely capacitive circuit, derive the expression for current drawn and power consumed. Draw the waveform of current voltage and power. **8**

b) A coil having resistance of 15Ω and inductance of 0.05 H is connected in series with $100 \mu\text{F}$ capacitor across 230 V , 50 Hz a.c. supply. Find :

i) The current taken

ii) The phase difference between supply voltage and current

iii) Voltage drop across the coil

iv) Voltage drop across the capacitor. **8**

OR

10. a) Sketch :

i) Impedance triangle

ii) Admittance triangle

Define admittance, susceptance and conductance as related to a.c. circuit.

How admittance is expressed in rectangular form ? **8**



b) Impedance of $(4 - j10)\Omega$ is connected in parallel with another impedance of $(6 + j8)\Omega$. The circuit is connected across 230 V, 50 Hz, single phase a.c. supply. Find :

i) Branch currents

ii) Total current

iii) Total power factor of circuit

iv) Power consumed by the circuit

v) Total impedance of the circuit.

8

11. a) Derive the expression for emf equation of single phase transformer. Hence write down the expression for transformation ratio.

6

b) A 1.5 KVA, 220/110 V, 50 Hz single phase transformer has iron loss of 32 W and full load copper loss of 44 W. Calculate % efficiency of transformer at

i) Full load 0.8 p.f. lag

ii) Full load unity p.f

iii) Half full load 0.8 p.f. lead.

6

c) State the relationship between line and phase values of voltage and current for 3 phase star connected load and delta connected load state the equation of active and reactive power consumed by 3 phase load.

6

OR



12. a) With neat diagram describe a test for finding out the efficiency and regulation of transformer by direct loading. **6**
- b) Three identical coils each having resistance of $15\ \Omega$ and inductance of $0.03\ \text{H}$ are connected in delta across 3 phase, $440\ \text{V}$, $50\ \text{Hz}$ supply. Calculate line current and power consumed by the load.
- If the same load is now connected in star across same supply. Calculate the power consumed by the load. **6**
- c) State different losses occurring in single phase transformer. Mention the part where each loss occurs. How these losses can be minimised ? **6**