

Total No. of Questions—8]

[Total No. of Printed Pages—3

| | |
|-------------|--|
| Seat No. | |
|-------------|--|

[4756]-103**F.E. (First Semester) EXAMINATION, 2015****BASIC ELECTRONICS ENGINEERING****(2012 PATTERN)****Time : Two Hours****Maximum Marks : 50**

- N.B. :-**
- (i) Figures to the right indicate full marks.
 - (ii) Neat diagrams must be drawn wherever necessary.
 - (iii) Use of electronic pocket calculator is allowed.
 - (iv) Assume suitable data, if necessary.


1. (a) Explain the working of positive clamper with its waveforms. [6]
- (b) What is dc load line ? Explain the role of Q-point on dc load line. [6]

Or

2. (a) Explain the working of positive biased shunt clipper with its input and output waveforms. [6]
- (b) Differentiate between CB, CE and CC configurations. [6]

P.T.O.

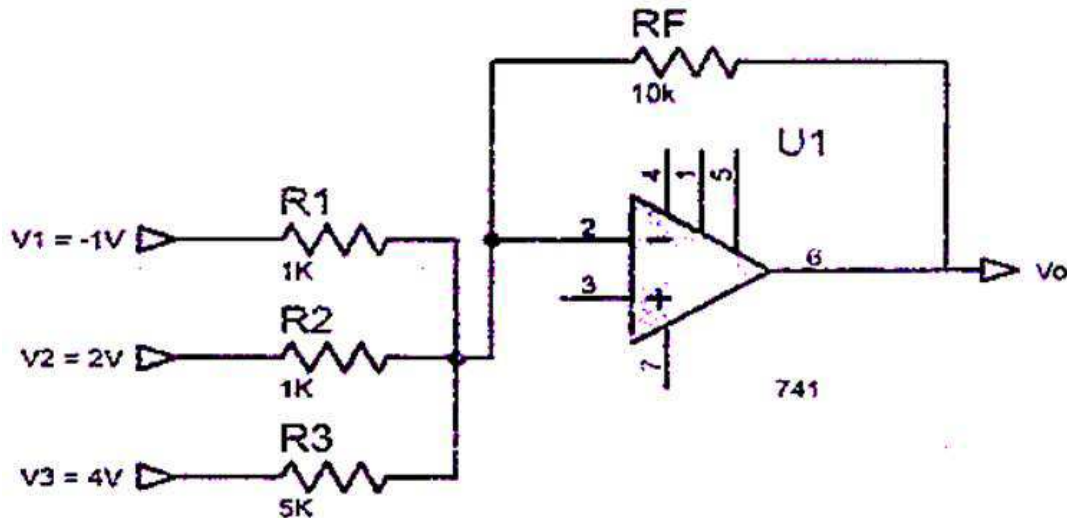3. (a) In shown in the following Fig. let $R_1 = R_2 = 1 \text{ k}\Omega$, $R_3 = 5 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$, $V_1 = -1\text{V}$, $V_2 = 2\text{V}$ and $V_3 = 4\text{V}$. Calculate V_o . [6]



- (b) State the IC number for the following two input logic gate : [6]
- (i) AND
 - (ii) NAND
 - (iii) OR
 - (iv) NOR
 - (v) EX-OR
 - (vi) NOT.

Or

4. (a) Define the following parameters of op-amp : [6]
- (i) BW
 - (ii) PSRR
 - (iii) CMRR.

- (b) Draw the explain full adder using two half adder with its truth table. [6]
5. (a) With a neat diagram explain the construction and working of LVDT. Give its advantages, disadvantages and applications. [7]
- (b) Draw a neat block diagram of a digital thermometer and explain its operation. [6]

Or

6. (a) Write a short note on Selection criterion for transducers. [7]
- (b) Compare : [6]
- (i) SCR and TRIAC
www.sppuonline.com
- (ii) DIAC and TRIAC.
7. (a) Draw and explain the electromagnetic spectrum or IEEE frequency spectrum. List its applications. [7]
- (b) Compare : AM and FM. [6]

Or

8. (a) What is modulation ? Explain AM technique in detail and write AM expression. [7]
- (b) Explain the basic structure of mobile phone system. [6]