

Total No. of Questions—12]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[4857]-153**S.E. (Electrical) (I Sem.) EXAMINATION, 2015****ANALOG AND DIGITAL ELECTRONICS****(2008 PATTERN)****Time : Three Hours****Maximum Marks : 100**

- N.B. :—** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6 from Section I and Q. No. 7 or Q. No. 8, Q. No. 9 or Q. No. 10, Q. No. 11 or Q. No. 12 from Section II.
- (ii) Answers to the two Sections should be written in separate answer-books.
- (iii) Neat diagrams must be drawn wherever necessary.
- (iv) Figures to the right indicate full marks.
- (v) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- (vi) Assume suitable data, if necessary.

SECTION I

1. (a) Draw and explain input and output characteristics of CB configuration. [8]
- (b) Draw and explain working of RC-coupled amplifier. [8]

Or

2. (a) Explain the drain characteristics of FET. [8]
- (b) Explain with neat circuit diagram working of Push Pull amplifier. [8]

P.T.O.

3. (a) Define the following terms related with operational amplifier and compare their values with those of ideal OPAMP : [8]
- (i) CMRR
 - (ii) Slew rate
 - (iii) PSRR
 - (iv) Input bias current.
- (b) What are the types of comparators ? Explain the operation of inverting comparator. Draw the input and output voltage waveform. [8]

Or

4. (a) Explain the circuit of voltage to current converter with floating load. Mention the field of applications. [8]
- (b) Explain OPAMP as : [8]
- (i) Instrumentation Amplifier
 - (ii) Integrator.
5. (a) Draw neat circuit diagram and explain OPAMP as sine wave generator. [9]
- (b) Draw and explain with frequency response curve first order low pass filter. [9]

Or

6. (a) Explain the operation of IC555 as an Astable Multivibrator. [9]
- (b) Draw the practical voltage regulator using IC LM 317 and justify the use of each component in the circuit. [9]

SECTION II

7. (a) Convert the following : [12]
- (i) What is the decimal equivalent of octal 314.734_{10} ?
 - (ii) Convert given number to Octal equivalent $1E7B_{16}$.
 - (iii) Convert the following binary number to Gray code 111011_{binary} .
 - (iv) Excess-3 code 111011_{binary} .
- (b) Perform the following operation : [6]
- (i) Add the following numbers $0FAC_H$ and $387F_H$
 - (ii) Subtract using 2's complement $125_{10} - 68_{10}$.

Or

8. (a) What is a comparator ? Design and draw a 1 bit comparator circuit using K-map. [9]
- (b) Draw and explain 8 : 1 Multiplexer circuit using 4 : 1 multiplexer. [9]
9. (a) Draw and discuss logic diagram of JK flip-flop and how to build T flip-flop using JK flip-flop. Write the truth tables for both. [8]
- (b) Explain 4 bit S I S 0 shift register and hence explain twisted ring counter. Draw timing diagram. [8]

Or

10. (a) What is the Modulus of counter ? Design a MOD-10 counter draw circuit diagram, truth table of 4 bit ripple counter. [8]
- (b) Design 1 : 4 De-multiplexer using K-map. [8]

- 11.** (a) Give the complete classification of memories. [8]
(b) Differentiate between Synchronous and Asynchronous counter.
Draw the circuit diagram of Synchronous counter using JK flip-flops. [8]

Or

- 12.** (a) Differentiate between Multiplexer and De-multiplexer with its applications. [8]
(b) Explain R-2R ladder Digital to Analog converter. [8]

www.sppuonline.com