

Total No. of Questions—12]

[Total No. of Printed Pages—6

Seat No.	
-------------	--

[5057]-65**S.E. (E&TC Engineering) (First Semester) EXAMINATION, 2016****POWER DEVICES AND MACHINES****(2008 PATTERN)****Time : Three Hours****Maximum Marks : 100**

N.B. :- (i) Answers to the two sections should be written in separate answer-books.

(ii) Neat diagrams and waveforms must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of non-programmable calculator is allowed.

(v) Assume suitable data, if necessary.

SECTION I

1. (a) Compare power MOSFET with IGBT ? [5]
- (b) Explain construction and steady state characteristics of power BJT. [7]
- (c) The reverse recovery time of a power diode is 5 μ s and rate of fall of diode current is 80 A/ μ s. If softness factor is 0.5, determine : [6]
 - (i) t_a & t_b
 - (ii) Peak inverse current (I_{RR})
 - (iii) Storage charge (Q_{RR})

P.T.O.

Or

2. (a) Compare power MOSFET with power BJT. [5]
- (b) What is latch up in IGBT ? Explain causes and remedies for latch up. [7]
- (c) Draw and explain Gate Drive Circuit for IGBT. [6]
3. (a) Draw two transistor analogy of SCR ? Derive an expression for its anode current I_A ? [6]
- (b) The gate triggering circuit of a SCR has a source voltage of 15 V and the gate cathode characteristics has a straight line slope of 130. If gate power dissipation is 0.5 W, calculate : [6]
- (i) Triggering voltage
- (ii) Triggering current
- (iii) Gate series resistance.
- (c) Compare SCR with GTO ? [4]

Or

4. (a) Compare SCR with TRIAC ? [5]
- (b) Explain construction and steady state characteristics of SCR. [6]
- (c) Draw and explain synchronized UJT triggering circuit for SCR with waveforms. [5]

5. (a) Explain single phase fully controlled rectifier for R-L load with various modes of operations and waveforms. Also derive expressions for average output voltage and rms output voltage. [10]
- (b) A single phase semi-converter is operated from 120 V, 50 Hz AC supply. The load resistance is 10Ω . If the average output voltage is 25% of the maximum possible average output voltage, determine : [6]
- (i) Firing angle
- (ii) Average output current
- (iii) rms output current.

Or

6. (a) A single phase full wave ac voltage controller has a resistive load of $R = 10 \Omega$ and the input voltage is $V_s = 230 \text{ V (rms)}$, 50 Hz. The delay angles of thyristors T1 and T2 are equal : $\alpha_1 = \alpha_2 = \pi/3$. Determine : [6]
- (i) the rms output voltage and current
- (ii) the input PF
- (iii) rms current of each SCR.
- (b) Draw and explain single phase full wave AC voltage controller for R load and derive an expression for its output voltage. Also draw the following waveforms : [10]
- (i) gate pulses

- (ii) output voltage
- (iii) output current
- (iv) voltage across SCR1
- (v) voltage across SCR2.

SECTION II

7. (a) What is a DC chopper ? Explain different control techniques in DC chopper. [7]
- (b) A step down DC chopper has a resistive load of $R = 15 \Omega$ and input voltage $V_s = 200 \text{ V}$. When the chopper remains ON, its voltage drop is 2.5 V . The chopper frequency is 1 kHz . If the duty cycle is 50% , determine : [6]
- (i) Average and rms output voltages
 - (ii) Chopper efficiency.
- (c) Explain with block schematic working of Off-line UPS. [5]

Or

8. (a) Single phase full bridge inverter has a resistive load of $R = 3 \Omega$, dc input voltage is 50 V . Calculate : [4]
- (i) rms o/p voltage at the fundamental frequency E_1
 - (ii) Output power P_0 .

(b) Explain $1 - \phi$ bridge inverter for R-L load with circuit and waveforms. Derive expression o/p rms voltage. [8]

(c) Explain step up chopper with circuit ? Show that : [6]

$$V_0 = \frac{V_s}{(1 - D)}.$$

9. (a) Explain construction, torque-speed and torque-current characteristics for dc shunt motor. [10]

(b) A 4-pole, lap wound DC motor has 500 conductors. Its speed is 1000 rpm. The flux per pole is 20 mWb. It is connected to 200 V dc supply, armature resistance is 0.8 Ω . Find : [6]

(i) Back e.m.f.

(ii) Armature current

(iii) Torque developed.

Or

10. (a) Explain torque-speed characteristics of 3-phase induction motor. [8]

(b) Explain construction, working and characteristics of ac servomotor. [8]

11. (a) Draw and explain various types of 3-phase transformer connection along with relation between phase and line voltages and currents. [8]

- (b) State various protection methods for motors ? Explain field failure protection method for dc motor in detail. [8]

Or

- 12.** (a) Explain construction, working and characteristics of BLDC motor. [8]
- (b) What are types of stepper motor ? Explain any *one* type with construction and working in detail. [8]

www.sppuonline.com