

Nov-Dec

2010

Total No. of Questions—12]

[Total No. of Printed Pages—4+2

[3862]-167**S.E. (E&TC) (Second Semester) EXAMINATION, 2010****INTEGRATED CIRCUITS AND APPLICATIONS****(2008 COURSE)****Time : Three Hours****Maximum Marks : 100**

N.B. :- (i) Answer *three* questions from Section I and *three* questions from Section II.

(ii) Answers to the two Sections should be written in separate answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(vi) Assume suitable data, if necessary.


SECTION I

1. (a) Which are the different configurations of differential amplifiers ?

Do the D.C. analysis of Dual-Input Balanced output differential amplifier to locate Q-point ? [8]

(b) Explain the working of current mirror circuit with neat circuit diagram and derive the expression for constant current. Justify why it is known as current mirror. [8]

P.T.O.

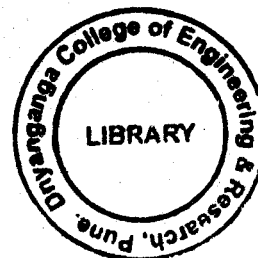

Or

2. (a) What is op-amp ? Draw its block diagram and explain the function of each block in detail. [8]
- (b) An emitter-biased dual-input balanced-output differential amplifier has the following specifications : $|V_{CC}| = |-V_{EE}| = 10 \text{ V}$, $R_{C1} = R_{C2} = 2.7 \text{ k}\Omega$ and $R_E = 5.6 \text{ k}\Omega$; the transistor array is CA3086 with $\beta_{a.c.} = \beta_{d.c.} = 100$ and $V_{BE} = 0.715 \text{ V}$. Calculate :
- (i) The voltage gain
- (ii) The input resistance
- (iii) The output resistance. [6]
- (c) Compare Ideal op-amp and practical op-amp. [2]
3. (a) In the op-amp circuit given in Fig. 1, find output offset voltage. Also find value of R_{comp} to compensate this output offset voltage. [6]

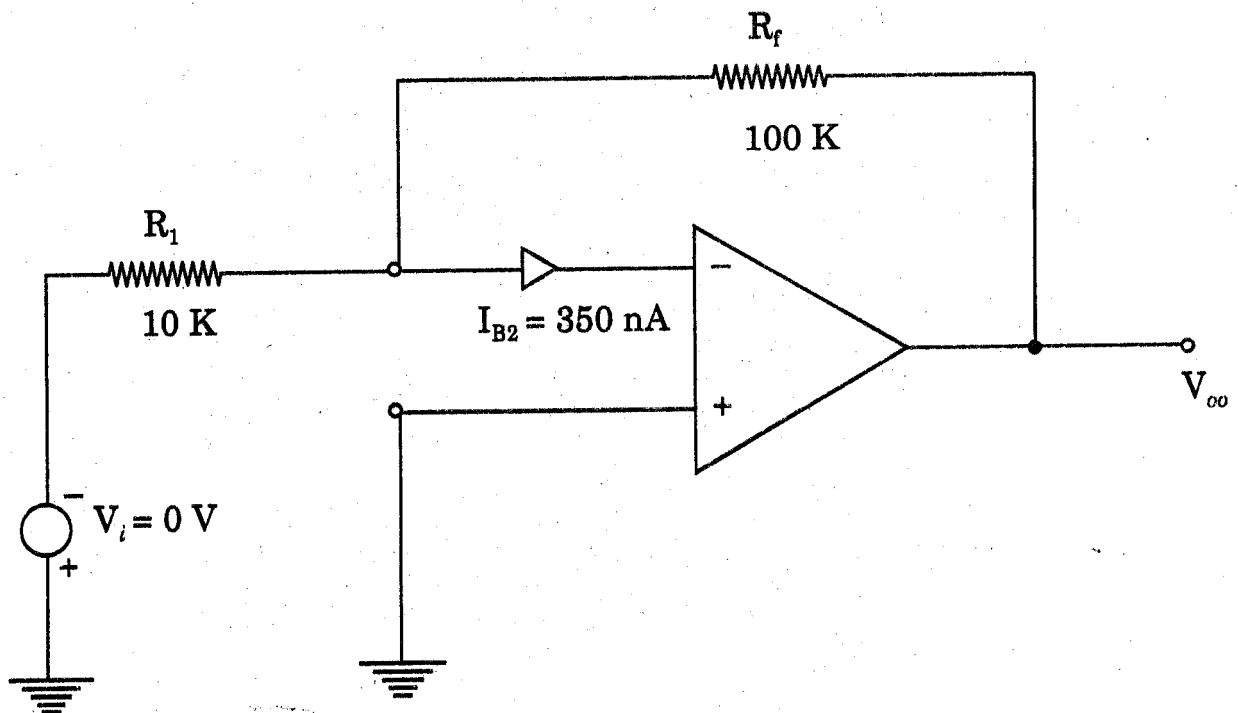


Fig. 1

- (b) Write a short note on frequency compensation in op-amps. [6]
- (c) What is CMRR ? Explain its significance in op-amp. [4]

Or

- 4. (a) Explain frequency dependence of loop gain using Bode plot. [8]
- (b) Which are the different types of noises that are associated with op-amps ? Draw op-amp. noise model and give expression for output noise voltage. [8]
- 5. (a) Which are the different techniques used to achieve non-linear amplification ? Explain in detail synthesized non-linear response with neat circuit diagram. [8]
- (b) Why basic integrator is needed to be modified ? Draw the circuit diagram of practical integrator along with frequency response and explain its operation. [6]
- (c) Write a short note on averaging circuit. [4]

Or

- 6. (a) With neat circuit diagram explain the operation of V to I converter with grounded load and give its application. [6]

- (b) Design a differentiator to differentiate an input signal whose frequency varies from 50 Hz to 2 kHz. [6]
- (c) Draw the circuit diagram of two op-amp. differential amplifier and explain its operation. [6]

SECTION II

7. (a) What is precision rectifier ? Explain the operation of precision full wave rectifier with neat circuit diagram. [8]
- (b) For the Inverting Schmitt Trigger given in Fig. 2, find V_{TH} , V_{TL} , ΔV_T and draw the input/output waveforms. [6]

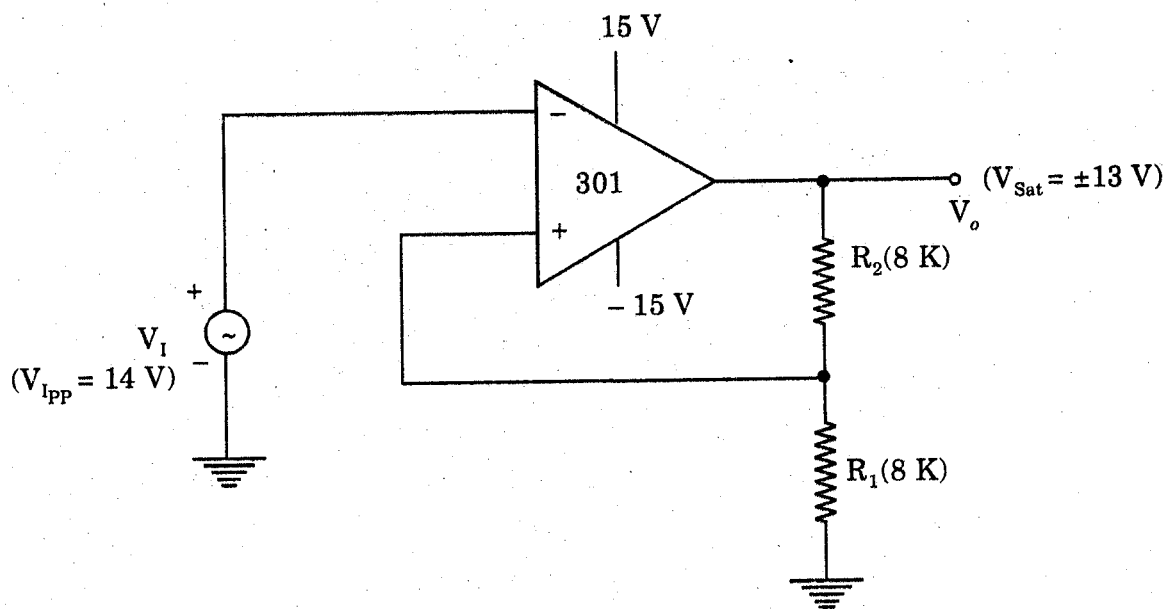


Fig. 2

- (c) Write a short note on IC LM317. [4]

8. (a) Draw the neat circuit diagram of Instrumentation Amplifier which amplifies output of a bridge which contains one resistive transducer. Derive the expression for output voltage. [8]
- (b) What is sample and hold amplifier ? Explain its operation with the help of circuit diagram. [6]
- (c) Explain operation of peak detector with the help of circuit diagram. [4]
9. (a) Draw the neat diagram of F to V converter and explain its operation. [8]
- (b) Explain the operation of successive approximation type ADC with neat block diagram. [8]

Or

10. (a) Explain in detail specifications of ADCs. [8]
- (b) Draw the circuit diagram of voltage mode R-2R ladder DAC and explain its working. [8]
11. (a) With the help of neat block diagram explain operation of PLL. Define the terms Lock range and Capture range. [8]
- (b) Write a short note on second order active Band Pass Filter. [8]

Or

12. Write short notes on any two :

[16]

- (a) Graphic equalizer
- (b) PLL as frequency synthesizer
- (c) FM Demodulator using PLL.

www.sppuonline.com

www.sppuonline.com