

UNIVERSITY OF PUNE

[4363]-183

T. E.(Electronics & Telecomm-Semester-I) Examination - 2013

NETWORK SYNTHESIS & FILTER DESIGN(304183)

(2008 Pattern)

[Total No. of Questions :]

[Total No. of Printed Pages :4]

[Time : 3 Hours]

[Max. Marks : 100]

Instructions :

- (1) Answer **any three** from each Section.
- (2) Answers to the **two sections** should be written in **separate answer-books**.
- (3) Black figures to the right indicate full marks.
- (4) Neat diagrams must be drawn wherever necessary.
- (5) Use of electronic pocket calculator is allowed.
- (6) Assume suitable data, if necessary.

SECTION –I


- Q.1 a) Define the terms causality & realizability state and explain the condition for stability of a network [6]
- b) What is positive real function? State the necessary and sufficient condition for a function to be positive real. [6]
- c) Test whether following polynomial are Hurwitz [6]
- i) $S^4 + S^3 + 4S^2 + 2S + 3$
- ii) $S^4 + S^3 + 5S^2 + 3S + 4$

OR

- Q.2 a) Explain the following removal operations [6]
- i) Removal of pole at $s = \infty$ from given function
- ii) Removal of pole at $s = 0$ from given function
- b) Test whether the following function are positive real [6]
- i) $F(s) = \frac{S^2 + 2S + 25}{s^2 + 5s + 16}$
- ii) $F(s) = \frac{3S^2 + 5}{s(s^2 + 1)}$

 c) A network shown in **figure1** has driving point impedance $Z(s)$ with the poles and zeros located at the following places. [6]

Poles at $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$ and zero at -1 . If $Z(0) = 1 \Omega$ Determine the values of component R, L and C.



Q. 3 a) State properties of L-C driving point impedance of admittance function [4]

b) Realize the following R-C driving point impedance function in [6]

i) Foster I form ii) Caner I form

$$Z(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

c) Identify the following R-C network function and synthesize the same. [6]

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

OR

Q.4 a) Identify the following network function with proper justification [6]

$$F(s) = \frac{2(s+2)(s+4)}{(s+3)(s+6)}$$

Synthesize the same using foster II form.

b) State properties of RL driving point impedance function. Draw and explain reactance curves for R-L network [4]

c) Synthesize the following L-C function using Cauer –I form [6]

$$Z(s) = \frac{s^2 + 10s^3 + 12s}{s^4 + 4s^2 + 3}$$

Q.5 a) What is meant by zeros of transmission? Determine ZOTs of the network shown in **figure 2** [4]




b) Synthesize the voltage ratio $\frac{V_2}{V_1} = \frac{s^2+1}{s^2+2s+1}$ as a constant resistance [6]

bridged T network terminated in a 1Ω resistor

c) State properties of transfer function. Obtain transfer function of two part network in terms of z parameters [6]

OR

 Q.6 a) State residue condition. Determine whether the residue condition holds for following network shown in **figure 3** [4]



b) Synthesize $Z_{21}(s) = \frac{2}{s^3 + 3s^2 + 4s + 2}$ into L-C ladder network with 1Ω termination. [6]

c) Realize the following voltage ratio transfer function using a constant resistance lattice network with 1Ω termination. [6]

$$\frac{V_2}{V_1} = \frac{4}{s+6}$$

SECTION – II

Q.7 a) State properties of a Butterworth filter obtain transfer function and realize third order normalized LPF Butterworth filter convert it into LPF with cut-off frequency $\omega_c = 10^4$ rad/sec and load impedance of 500Ω [12]

b) Write short note on frequency Transformation [6]

OR


- Q.8 a) Synthesize a chebysher LPF to meet following specifications [18]
 i) Load resistance 600Ω
 ii) $\frac{1}{2}$ db ripple with pass bond
 iii) Cut-off frequently 5×10^5 rad/sec
 iv) At 1.5×10^6 rad/ see magnitude must be down 30 db.
- Q.9 a) Explain with suitable example the coefficient matching technique for obtaining element values. [8]
 b) Explain the position feedback topology used in active filter design and obtain it's transfer function. [8]

OR

- Q.10 a) Synthesize the following HPF function using RC-CR transformation on sullen key LPR [8]

$$H_{HP}(s) = K \frac{s^2}{s^2 + s + 25}$$

 - b) Write short note on [8]
 i) FDNR ii) Gyrator
- Q.11 a) What is multi element deviation ? Define variability and device expression for per unit change in parameter p due to simultaneous variation in all element [8]
- b) For the network shown in **figure 4** determine the transfer function V_o/I_{in} and compute sensitivity of Q_p , W_p and k with respect to the passive element R, L, C. (8) [8]



OR

- Q.12 a) Discuss the effect of parameter of OP-AMP on the performance of active filters. [8]
 b) Explain the concept of gain sensitivity. Explain the various factors affecting gain sensitivity [8]