

Total No. of Questions—4]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5316]-106

S.Y. B.Sc. (Computer Sc.) (I Sem.) EXAMINATION, 2018

ELECTRONICS

Paper II

(ELC-212 : Analog Systems)

(2013 PATTERN)

Time : Two Hours

Maximum Marks : 40

N.B. :— (i) All questions are compulsory.

(ii) Figures to the right indicate full marks.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Use of calculator is allowed.

1. Answer the following questions in *one* or *two* sentences each : [10×1=10]

(a) What do you mean by PIR sensor ?

(b) What do you mean by active sensor ?

(c) How many comparators are required for 3-bit flash ADC ?

(d) Find output voltage of LM-35 at 70°C.


(e) Find cut-off frequency of low pass filter if $R = 1 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$.

(f) Give any *two* applications of tilt sensor.

(g) Write any *two* salient features of instrumentation amplifier.

P.T.O.

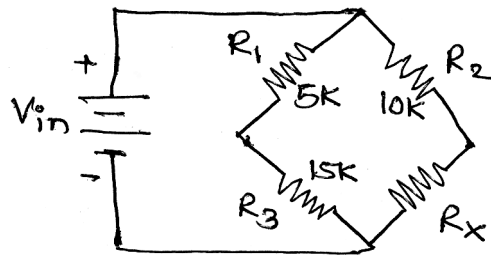- (h) Define accuracy w.r.t. ADC.
- (i) Write any *two* advantages of R-2R Ladder DAC.
- (j) Find unknown resistance R_x in balanced condition for the following figure :



2. Attempt any *two* of the following : [2×5=10]
- (a) A 4-bit R-2R ladder network with 0 = 0V and 1 = 10 V.
Find :
 - (i) Full scale output voltage
 - (ii) Analog output for digital input 1001
 - (iii) Analog output due to LSB change.
 - (b) Explain operating principle of LVDT with neat diagram.
 - (c) Differentiate between active and passive filters.
3. Attempt any *two* of the following : [2×5=10]
- (a) Draw circuit diagram of voltage to frequency converter and explain its operation.
 - (b) Explain with diagram the case study of ECG.
 - (c) Explain the working principle of capacitive touch sensor and state any *two* applications of it.

4. Attempt any *one* of the following : [1×10=10]

- (A) (i) Explain with neat diagram, principle of operation of pH sensor.
- (ii) Explain the working of successive approximation ADC with neat diagram.

Or

- (B) (i) Explain with neat diagram water level indicator system using float switch.
- (ii) Draw the circuit diagram of instrumentation amplifier using 3 op-amp. Derive an expression for output voltage.