

Total No. of Questions : 4]

SEAT No. :

[Total No. of Pages : 2

P643

[5315] - 124

S.Y. B.Sc.

ELECTRONIC SCIENCE

EL-212 : Digital Circuit Design

(2013 Pattern) (Paper - II) (Semester-I)

Time : 2 Hour]

[Max. Marks : 40

Instructions to the candidates:

- 1) *All questions are compulsory.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right indicate full marks.*

Q1) Answer All of the following:

- a) Write excitation table for J-K flipflop. [1]
- b) What is steady state accuracy test for digital to analog converter? [1]
- c) What do you mean by octet in K-map? [1]
- d) State the nature of input and output in case of thumb wheel switch. [1]
- e) Draw K-map for following equation
$$Y = \overline{A}\overline{B}C + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}.$$
 [2]
- f) “Non multiplexed display system draws large current from the power supply”. Comment. [2]
- g) “Flash type ADC is fastest ADC”. Comment. [2]
- h) State various methods for sequence generator. [2]

Q2) Attempt any Two of the following:

- a) Using K- map design 3-bit odd parity generator. [4]
- b) With the help of diagram explain the working of counter type ADC. [4]
- c) Draw a logic diagram and timing diagram of asynchronous decade counter using J-K flipflop. [4]

P.T.O.

