

Total No. of Questions—5]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[5116]-6

F.Y. B.Sc. (Computer Science) EXAMINATION, 2017

ELECTRONICS

Paper-II

(ELC-102 : Principles of Digital Electronics)

(2013 PATTERN)

Time : Three Hours

Maximum Marks : 80

N.B. :— (i) *All* questions are compulsory.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

1. Attempt *all* of the following :

[8×2=16]

- (a) Give the radix of binary and hexadecimal number system.
- (b) Simplify $y = ABC + AB$ using rules of Boolean algebra.
- (c) Find one's complement of $(9D)_{16}$.
- (d) How many control lines are required for 256 : 1 multiplexer ?
- (e) What do you mean by modulus of a counter ?
- (f) Write the truth table of tristate inverter.
- (g) Draw the logic symbol for positive edge triggered D-Flip-Flop and negative level triggered RS-Flip-Flop.
- (h) Distinguish between decoder and demultiplexer.

P.T.O.

2. Attempt any *four* of the following : [4×4=16]

- (a) With neat logic diagram explain the working of parity generator.
- (b) Construct all basic gates using NOR gates.
- (c) With neat logic diagram explain the working of full subtractor.
- (d) Perform the following :

(i) $(110111)_2 \equiv (?)_{\text{Gray}}$

(ii) $(875)_{10} \equiv (?)_{16}$

- (e) Convert the given SOP into standard form

$$y = A\bar{B} + \bar{C}$$


- (f) Subtract the following using 2's complement method.

$$(10001)_2 - (11100)_2$$

Comment on the result.

3. Attempt any *four* of the following : [4×4=16]

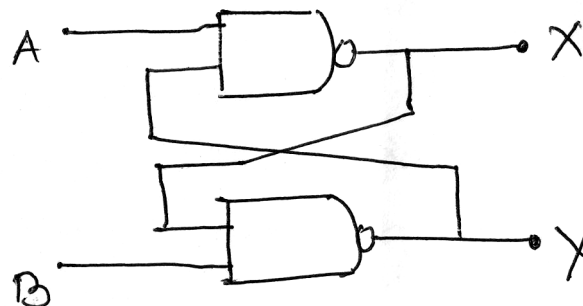- (a) Draw logic diagram for decimal to BCD converter. Write the truth table for the same.
- (b) Explain the working of the following circuit.




- (c) Explain the working of CMOS inverter with neat diagram.

- (d) With neat diagram explain working of 3-bit left shift serial in serial out shift register.
- (e) Explain the working of common cathode 7-segment display. Display 1 and 5 decimal numbers using common cathode 7-segment display.
- (f) Define the following parameters :
 - (i) Power Dissipation
 - (ii) Noise Margin
 - (iii) Switching Speed
 - (iv) Fan out.

4. Attempt any *four* of the following : [4×4=16]

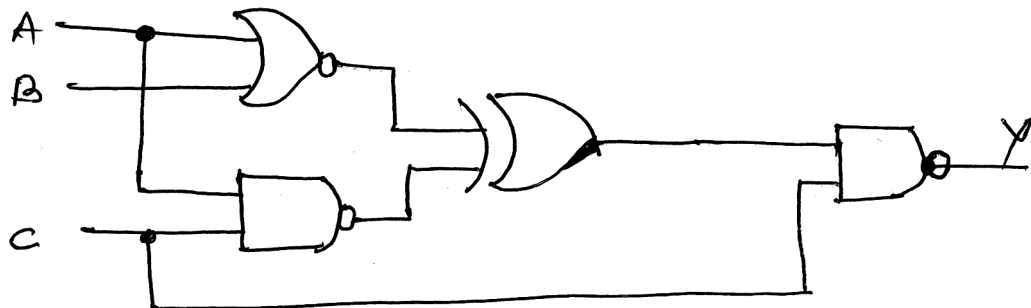- (a) Draw logic diagram of EX-OR gate and explain its working.
- (b) Write the truth table for the given circuit.



- (c) Explain block diagram of ALU.
- (d) Explain working of 4 : 1 multiplexer using NAND-NAND logic.
- (e) Explain working of 3-bit asynchronous down counter.
- (f) Show how IC 7490 can be connected for the following operation :
 - (i) MOD 7
 - (ii) MOD 3.

5. Attempt any *two* of the following : [2×8=16]

(A) (a) Convert the following :

(i) $(1101111)_2 \equiv (?)_{16}$

(ii) $(527)_{10} \equiv (?)_{\text{Excess-3}}$

(b) Simplify the Boolean expression using K-maps :

$$y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + ABC$$

Draw simplified diagram.

(B) (a) Explain the working of 2 bit digital comparator.

(b) Implement the following logic using multiplexer :

$$y = \bar{A}\bar{B}\bar{C}\bar{D} + ABCD + A\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D}$$

(C) (a) Explain working of 3×4 matrix keyboard encoder.

(b) What is race around condition ? Which Flip-Flop exhibits this condition ? How can race around condition be eliminated ?